 


Wave-form for question #1



Code for question #1:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity question1 is
    port (a : in std_logic_vector(3 downto 0);
          s : in std_logic_vector (2 downto 0);
          f : out std_logic_vector (3 downto 0)
        );
end entity;

architecture myarch of question1 is
    signal ouputShift : std_logic_vector(3 downto 0);
    signal outputInc   : std_logic_vector(3 downto 0);

    signal a_bitvector : bit_vector (3 downto 0);
    signal a_reverse    : std_logic_vector (3 downto 0);

begin
    --temporary signal assignments
    a_bitvector <= to_bitvector(a);

    loop1: for i in a'range generate
        a_reverse(a'high - i) <= a(i);
    end generate;

    --shift block
    with s(1 downto 0) select
        ouputShift <= to_stdlogicvector(a_bitvector srl 1) when "00",
                     to_stdlogicvector(a_bitvector sll 2) when "01",
                     a when "10",
                     a_reverse when others;

    --incrementer block
    with s(1 downto 0) select
        outputInc <= a+1 when "00",
                    a-1 when "01",
                    a+2 when "10",
                    (Others=>'Z') when others;

    --2-to-1 mux block
    with s(2) select
        f <= outputInc when '1',
            ouputShift when others;

end architecture;
```

Wave-form for question #2



Code for question #2:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity question1 is
    generic (n: integer := 5);
    port (a : in std_logic_vector(n-1 downto 0);
          s : in std_logic_vector (2 downto 0);
          f : out std_logic_vector (n-1 downto 0)
        );
end entity;

architecture myarch of question1 is
    signal ouputShift : std_logic_vector(n-1 downto 0);
    signal outputInc   : std_logic_vector(n-1 downto 0);

    signal a_bitvector : bit_vector (n-1 downto 0);
    signal a_reverse    : std_logic_vector (n-1 downto 0);

begin
    --temporary signal assignments
    a_bitvector <= to_bitvector(a);

    loop1: for i in a'range generate
        a_reverse(a'high - i) <= a(i);
    end generate;

    --shift block
    with s(1 downto 0) select
    ouputShift <= to_stdlogicvector(a_bitvector srl 1) when "00",
                  to_stdlogicvector(a_bitvector sll 2) when "01",
                  a when "10",
                  a_reverse when others;

    --incrementer block
    with s(1 downto 0) select
    outputInc <= a+1 when "00",
                 a-1 when "01",
                 a+2 when "10",
                 (Others=>'Z') when others;

    --2-to-1 mux block
    with s(2) select
    f <= outputInc when '1',
        ouputShift when others;

end architecture;
```

Test-bench for question #2:

```
library ieee;
use ieee.std_logic_1164.all;

entity test_question1 is
end;

architecture bench of test_question1 is
constant n: positive:=5;
component question1
    generic (n: integer := n);
    port (a : in  std_logic_vector(n-1 downto 0);
          s : in  std_logic_vector (2 downto 0);
          f : out std_logic_vector (n-1 downto 0)
    );
end component;

signal a : std_logic_vector (n-1 downto 0);
signal s : std_logic_vector (2 downto 0);
signal f : std_logic_vector (n-1 downto 0);

begin
a    <= "X1010",
      "X1111" after 10ns,
      "XZZZZ" after 20ns,
      "X1Z0X" after 30ns,

      "00011" after 40ns,
      "00000" after 50ns,
      "01000" after 60ns,
      "XXXXX" after 70ns;

s    <=
      "000",          -- f=a shift right
      "001" after 10ns, -- f=a shift left 2 units
      "010" after 20ns, -- f=a unchanged
      "011" after 30ns, -- f=a reverse bits
      "100" after 40ns, -- f=a+1
      "101" after 50ns, -- f=a-1
      "110" after 60ns, -- f=a+2
      "111" after 70ns; -- f=ZZZZZ
m: question1 port map (a,s,f);

end bench;
```